

Measurements Report



Avo Project

Students Data	
الاسم	الرقم الجامعي
1-عمر محمد حسن السيد	23011933
2-علي محمود علي	23010594
3-عبد الرحمن علي عبد الله	23010531
4-عمرو أحمد إبراهيم	23010624
5-عمر محمد محمود	23010621

Content

1. Overview.....	(3)
2. Simulation.....	(5)
A)Voltameter.	
B)Ammeter.	
C)Ohmmeter.	
D)Cap.meter.	
E)Continuity test.	
3. Code.....	(10)
4. Hardware.....	(13)

1. Overview

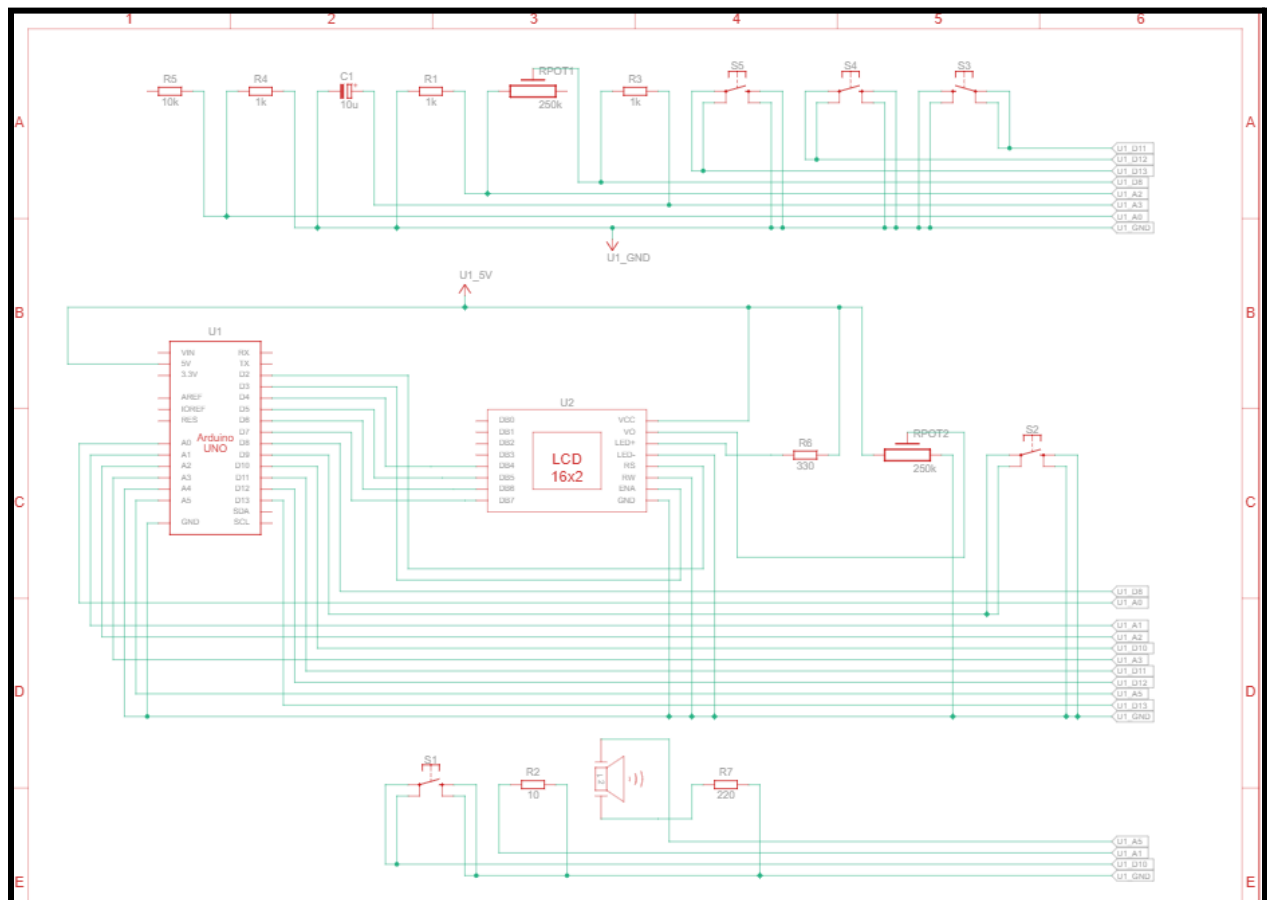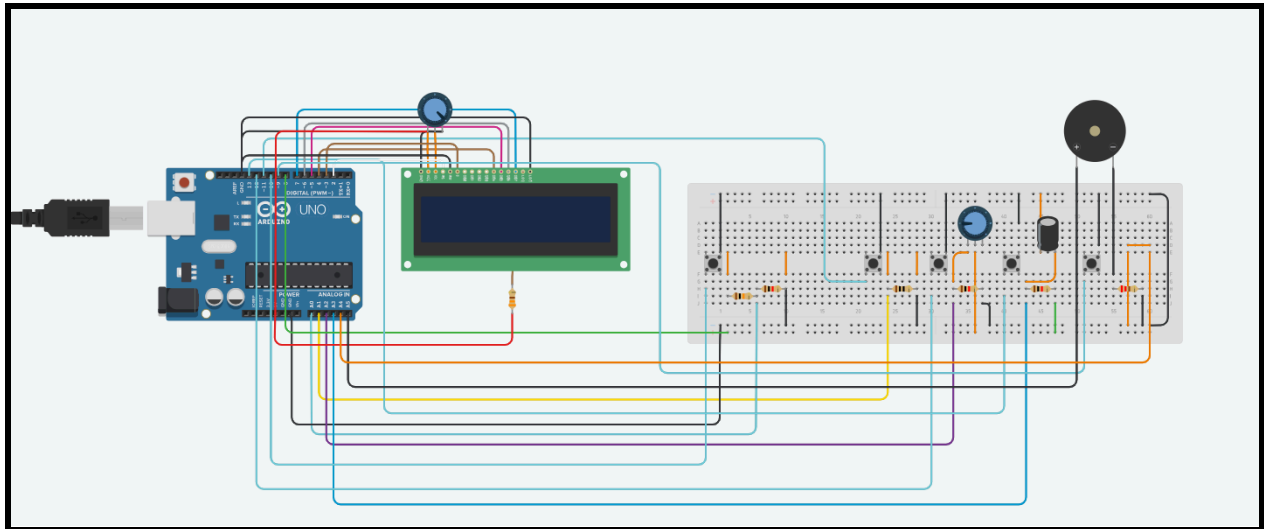

-A **digital multimeter**, often abbreviated as **DMM** or sometimes called a digital Avometer, is a versatile electronic tool used by technicians, engineers, and hobbyists to measure various electrical properties accurately.

Here's a brief overview of how it works and what it can measure:

1. Voltage (Volts): One of the primary functions of a digital multimeter is measuring voltage. It can measure both direct current (DC) and alternating current (AC) voltage levels. This capability allows users to check the voltage of batteries, power supplies, circuits, and electrical outlets.

2. Current (Amperes): Another crucial function is measuring current. Like voltage, it can measure both DC and AC currents. By breaking and connecting the circuit in series, the multimeter can measure the flow of electrical current through the circuit, helping users assess the current drawn by various components or devices.


3. Resistance (Ohms): Digital multimeters can also measure resistance. This feature is useful for diagnosing electrical faults, identifying open or short circuits, and determining the continuity of wires and components. By connecting the multimeter leads across the component or circuit under test, it measures the resistance in ohms.

4.Cap.meter(farad): measures a capacitor's ability to store charge, expressed in **farads (F)**. It applies a known voltage or current and calculates capacitance based on the response. These meters are used for checking, diagnosing, and designing electronic circuits. Accurate measurement usually requires discharging the capacitor first.

5.Continuity test: A continuity test with buzzer checks if an electrical path is complete. Using a multimeter set to continuity mode, the device emits a **beep** (buzzer sound) when the circuit is complete, indicating very low resistance. It's a fast and easy way to find broken wires, bad connections, or faulty components.

2.Simulation

A)Voltmeter:

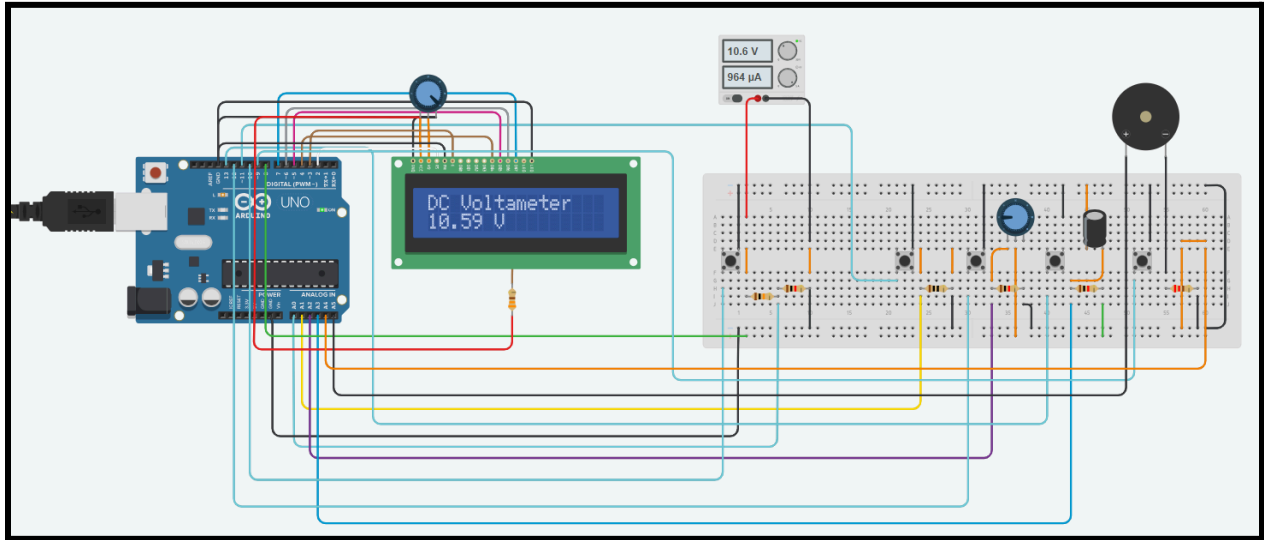


-A **voltmeter** is a device that can measure both **voltage** in the circuit. In this setup, an **Arduino** acts as a voltmeter by using its analog pins. To measure voltage, it reads the analog input (0–5V, scaled with a voltage divider). To measure current, it detects the voltage across a **series resistor**. By combining both measurements, the Arduino can function as a simple voltmeter.

- Here How the Voltmeter Works:

1. **Reads voltage** from pin **A0**, which is connected to a **voltage divider**.
2. The voltage divider steps down the input voltage using two resistors:
$$V_{in} = V_{out} \times (R1 + R2) / R2$$

(where $R1 = 10k\Omega$, $R2 = 1k\Omega$)
3. `analogRead()` measures V_{out} (0–5V), and the code scales it to get the original voltage (V_{in}).

B)Ammeter:

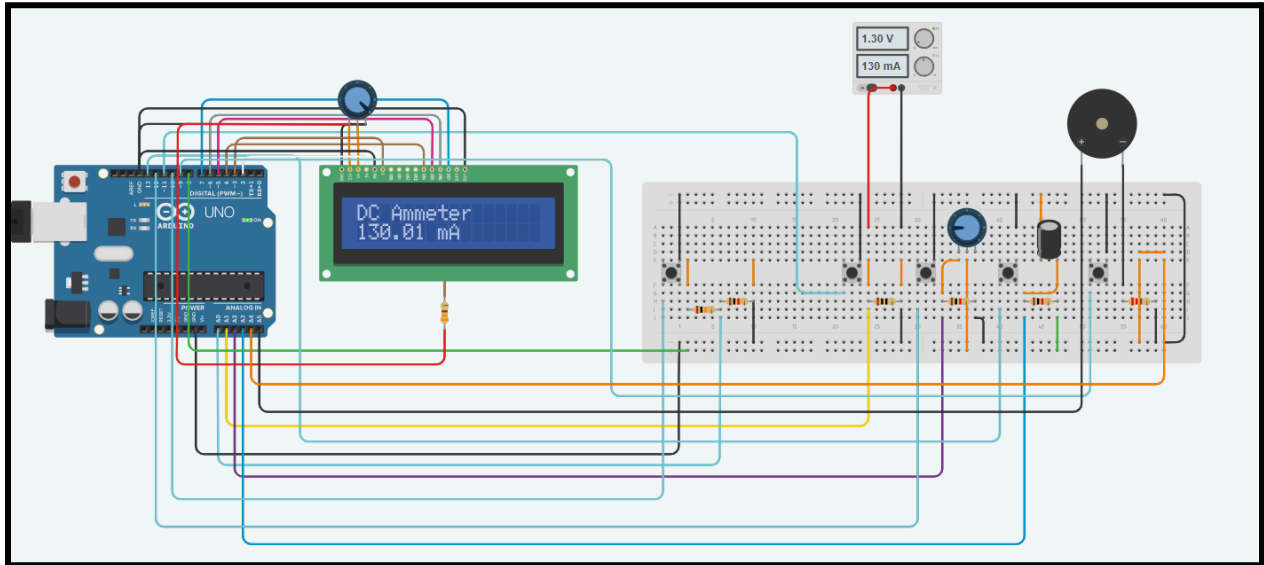


-An **ammeter** is a device used to measure the **electric current** flowing through a circuit. In this setup, the ammeter is connected to an **Arduino**. Since Arduino's analog pins measure voltage (0–5V), a **shunt resistor** (a low-resistance resistor) is placed in series with the circuit. The voltage drop across the shunt is measured and, using **Ohm's law** ($I = V/R$), the current is calculated. By selecting the value of the shunt resistor carefully, we can control the range of current that can be accurately measured.

-Here How the Ammeter Works:

1. **Reads voltage** across a **shunt resistor (10Ω)** from analog pin **A1**.
2. Uses Ohm's Law:
$$I = V/R$$

So:
$$\text{Current} = (V_{\text{out}}/10) \times 1000 \text{ mA}$$
3. `analogRead()` measures the voltage drop (`V_out`) across the shunt resistor, then converts it to current.

C) Ohmmeter:

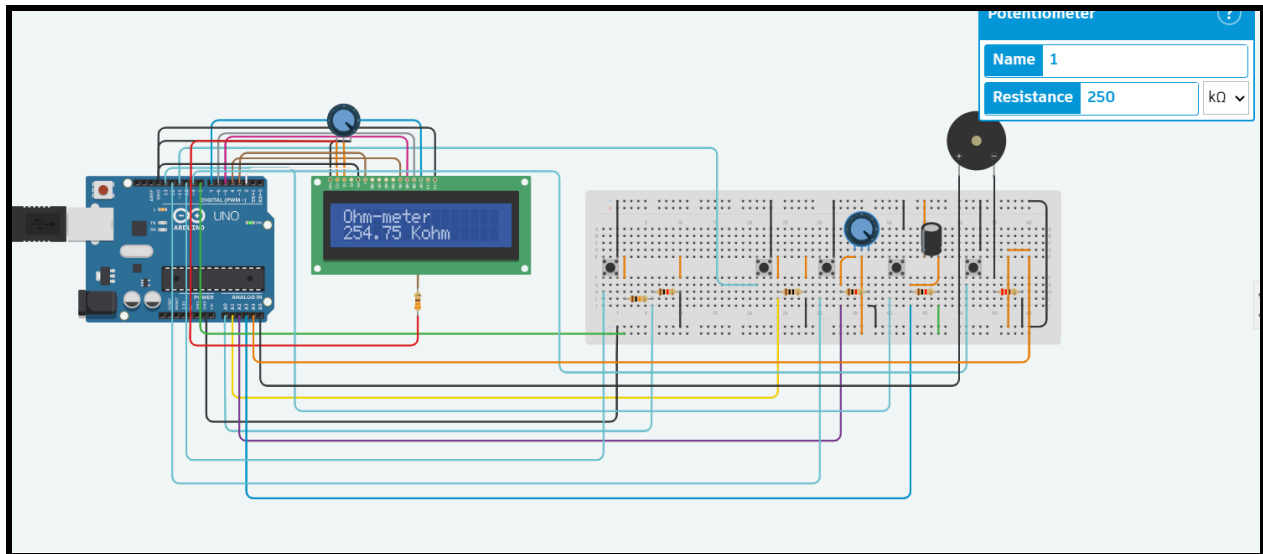


-An **ohmmeter** measures the **resistance** of a component. In this setup, an **Arduino** acts as an ohmmeter by applying a known voltage across the unknown resistor and measuring the resulting current or voltage drop. Using **Ohm's Law** ($R = V/I$), the resistance is calculated. Often, a **voltage divider** is used where the unknown resistor and a known resistor are connected in series, and Arduino measures the voltage across one of them to find the unknown resistance.

-Here How the Ohmmeter Works:

1. **Applies 5V** across a **known resistor (1kΩ)** in series with the **unknown resistor**.
2. Measures voltage drop across the **known resistor** at pin **A2**.
3. Calculates current:
$$I = V_{known}/R_{known}$$
4. Uses Ohm's Law to find the unknown resistance:
$$R_{unknown} = V_{known}/I = (5 - V_{known})/I$$
5. Displays result in ohms or kilo-ohms.

D)Cap.meter:

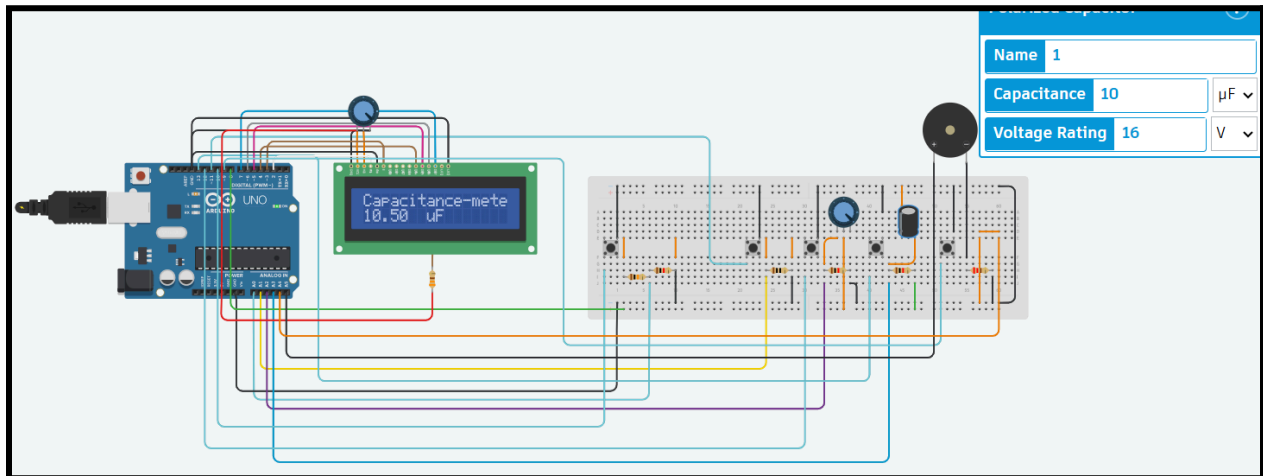


-A **capacitance meter (cap meter)** measures the **capacitance** of a capacitor. In this setup, an **Arduino** can act as a cap meter by charging the capacitor through a resistor and measuring the **time constant** (how fast the voltage rises). Using the formula $Vt = Vmax(1 - e^{-t/rc})$, the Arduino calculates the capacitance. This method depends on the known resistor value and the timing accuracy of the Arduino.

-Here How the Capacitance Meter Works:

1. **Discharges** the capacitor (sets pin **A3** LOW).
2. **Starts charging** the capacitor through a resistor when **VCC** is set HIGH.
3. Measures the **time** it takes for voltage at pin **A3** to reach ~63.2% of 5V ($\approx 3.16V$, or ADC value 646).
4. Uses the RC time constant formula:
$$Vt = Vmax(1 - e^{-t/rc})$$
5. Solves for capacitance:
$$C = t/R \text{ (Here, } R \text{ is assumed known } = 1K\Omega)$$

E)Continuity test:

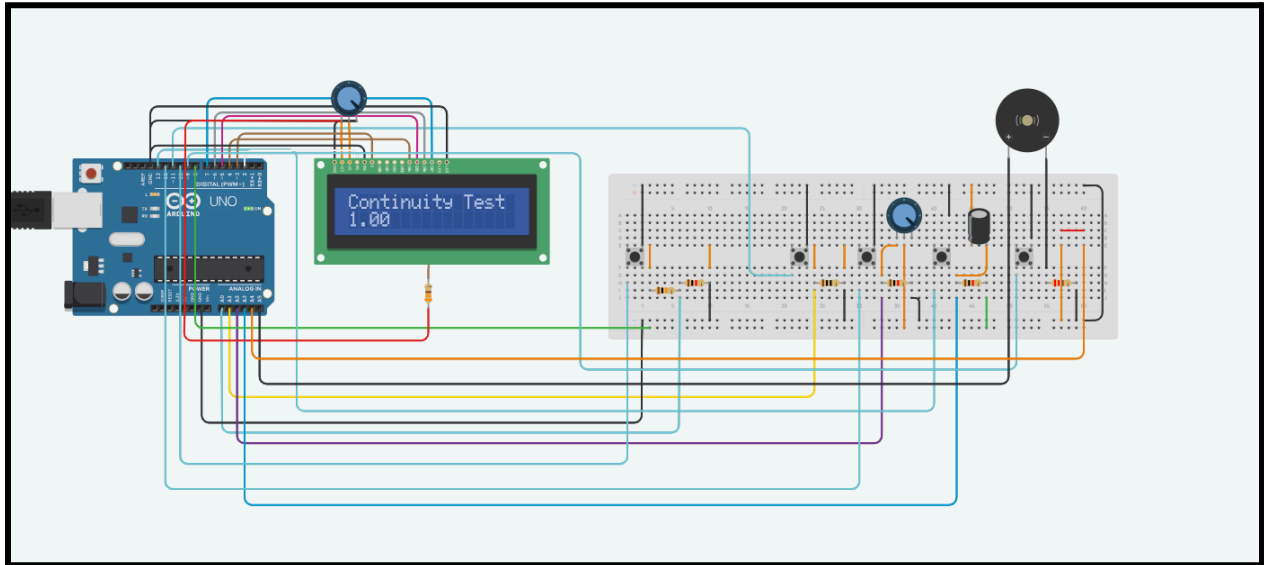

-The continuity test is a simple yet essential method used to check if there is a complete electrical connection between two points in a circuit. It works by connecting two probes to the points being tested; if the circuit is closed. This technique is commonly used to detect broken wires, faulty connections, or damaged circuit paths. When the circuit is closed, or a buzzer sounds to indicate a successful connection.

-Here How the Continuity Tester Works:

1. **Reads** pin **A4** (defined as **probe**) to detect electrical connection.
2. If the pin reads **LOW**, it means the circuit is closed (i.e., there's continuity).
3. Then it:
 - **Activates a buzzer** using **tone()** on pin **A5**
 - **Displays "1"** on the LCD
4. If the pin reads **HIGH** (open circuit), the buzzer is off and "0" is shown.

3.Code

```
1  #include <LiquidCrystal.h>
2
3  #define Voltage_Divder_Volt A0
4  #define ammeterVolt A1
5  #define readed A2
6  #define capacitor A3
7  #define probe A4
8  #define buzzer_sound A5
9
10
11 #define RS 2
12 #define EN 3
13 #define D4 4
14 #define D5 5
15 #define D6 6
16 #define D7 7
17
18 LiquidCrystal lcd(RS, EN, D4, D5, D6, D7);
19
20
21 //Resistors
22 #define Shunt_Resistance 10
23 #define Series_Resistance 1
24 #define Ammeter_Resistance 0.01
25
26 int switch5 = 9;
27 int Switch1 = 10;
28 int Switch2 = 11;
29 int Switch3 = 12;
30 int Switch4 = 13;
31 int VCC = 8 ;
```

```
33 int Active_Device = 0 ;
34
35
36 int Pressed_Button() {
37     for (int i = 9 ; i < 14 ; i++) {
38         if (digitalRead(i) == LOW) {
39             return i;
40         }
41     }
42     return -1;
43 }
44
45
46 void setup() {
47     Serial.begin(9600);
48     pinMode(Voltage_Divder_Volt, INPUT);
49     pinMode(ammeterVolt, INPUT);
50     pinMode(readed, INPUT);
51     pinMode(Switch1, INPUT_PULLUP);
52     pinMode(Switch2, INPUT_PULLUP);
53     pinMode(Switch3, INPUT_PULLUP);
54     pinMode(Switch4, INPUT_PULLUP);
55     pinMode(switch5, INPUT_PULLUP);
56     pinMode(probe, INPUT_PULLUP);
57     pinMode(buzzer_sound, OUTPUT);
58     pinMode(VCC , OUTPUT) ;
59     digitalWrite(VCC , LOW );
60     lcd.begin(16, 2);
61
62
63 }
64
```

```
65 void Print_Reading(String Device , float Reading , String Unit , int Fraction_Num = 2 ) {
66     lcd.clear(); // clear previous output
67     lcd.setCursor(0, 0);
68     lcd.print(Device);
69
70     lcd.setCursor(0, 1);
71     lcd.print(Reading, Fraction_Num); // Print float with 2 decimal places
72     lcd.print(" ");
73     lcd.print(Unit);
74 }
75
76 void WelcomeMessage(){
77     lcd.clear(); // clear previous output
78     lcd.setCursor(0, 0);
79     lcd.print("Measure Project");
80     lcd.setCursor(0, 1);
81     lcd.print("AVO METER");
82 }
83
84
85
86 void voltmeter() {
87     float voltOut = (analogRead(Voltage_Divder_Volt) * 5.0)/1023;
88     float voltIn = voltOut * (Shunt_Resistance + Series_Resistance) / Series_Resistance;
89     Serial.print("The voltage = ");
90     Serial.print(voltIn);
91     Serial.println(" V");
92     Print_Reading("DC Voltameter" , voltIn , "V");
93 }
```

```

95 void ammeter() {
96     int val = analogRead(ammeterVolt);
97     float voltOut = (val * 5.0)/1023;
98     float current = (voltOut / Ammeter_Resistance);
99     Serial.print("The Current = ");
100     Serial.print(current);
101     Serial.println(" mA");
102     Print_Reading("DC Ammeter" , current ,"mA");
103 }
104
105 void ohmmeter() {
106     digitalWrite( VCC , HIGH);
107     int val = analogRead(readed);
108     float volt = (val * 5.0) / 1023.0;
109     float volt_across_unknown = 5.0 - volt;
110     float current = volt / 1000.0;
111     float res = volt_across_unknown / current;
112     Serial.print("resistance = ");
113     Serial.print(res);
114     Serial.println(" ohm");
115     digitalWrite( VCC , LOW);
116     if (res > 1000) {
117         Print_Reading("Ohm-meter" , res/1000 ,"Kohm");
118     }
119     else {
120         Print_Reading("Ohm-meter" , res ,"Ohm");
121     }
122 }
123
124 }

```

```

126 void capacitance_meter() {
127     float cap = 0;
128     long start_time = 0;
129     long time_interval = 0;
130
131     pinMode(capacitor, OUTPUT);
132     digitalWrite(capacitor, LOW);
133     delay(500);
134
135     pinMode(capacitor, INPUT);
136     start_time = micros();
137     digitalWrite(VCC, HIGH);
138     while (analogRead(capacitor) < 646) {}
139
140     time_interval = micros() - start_time;
141     cap = (float)time_interval / 1000.0;
142
143     Serial.print("capacitance = ");
144     Serial.print(cap);
145     Serial.println(" uF");
146     digitalWrite(VCC, LOW);
147     Print_Reading("Capacitance-meter" , cap ," uF");
148     delay(200);
149 }
150
151
152 void buzzer()
153 {
154     int state = 0;
155     state = digitalRead(probe);
156
157

```

```

158     if (state == LOW) {
159         tone(buzzer_sound, 985);
160         Print_Reading("Continuity Test" , 1 ," ");
161     }
162     else {noTone(buzzer_sound);Print_Reading("Continuity Test" , 0 ," ");}
163     delay(100);
164 }
165
166
167
168 void loop() {
169
170     int newPressed = Pressed_Button();
171     if (newPressed != -1 && newPressed != Active_Device) {
172         Active_Device = newPressed;
173     }
174
175
176
177     switch (Active_Device) {
178     case 9:
179         Serial.println("Now buzzer");
180         buzzer();
181         break;
182
183     case 10:
184         noTone(buzzer_sound);
185         Serial.println("Now Voltmeter");
186         voltmeter();
187         break;
188

```

```
189
190     case 11:
191         noTone(buzzer_sound);
192         Serial.println("Now Ammeter");
193         ammeter();
194         break;
195
196     case 12:
197         noTone(buzzer_sound);
198         Serial.println("Now Ohmmeter");
199         ohmmeter();
200         break;
201
202     case 13:
203         noTone(buzzer_sound);
204         Serial.println("Now Capacitance");
205         capacitance_meter();
206         break;
207
208     default:
209         WelcomeMessage();
210         noTone(buzzer_sound);
211         break;
212 }
213
214 delay(50) ;
215 }
216
```